



Faculty of Enigeering



Cairo University

Analog Electronics **Project # 1**

Design and Implementation of a Biquad

Presented for **ELC 3060** Cadence Project

Presented to:

Dr. Mohammed Mobarak


T.A: Mohammed Ramadan

(3rd Year Electronics and Electrical Communication Engineers)

مجدي أحمد عباس عبد الحميد الابرق

Sec: 3 / I.D: 9210899 / BN: 36

UNIVERSAL BIQUADRATIC FILTER

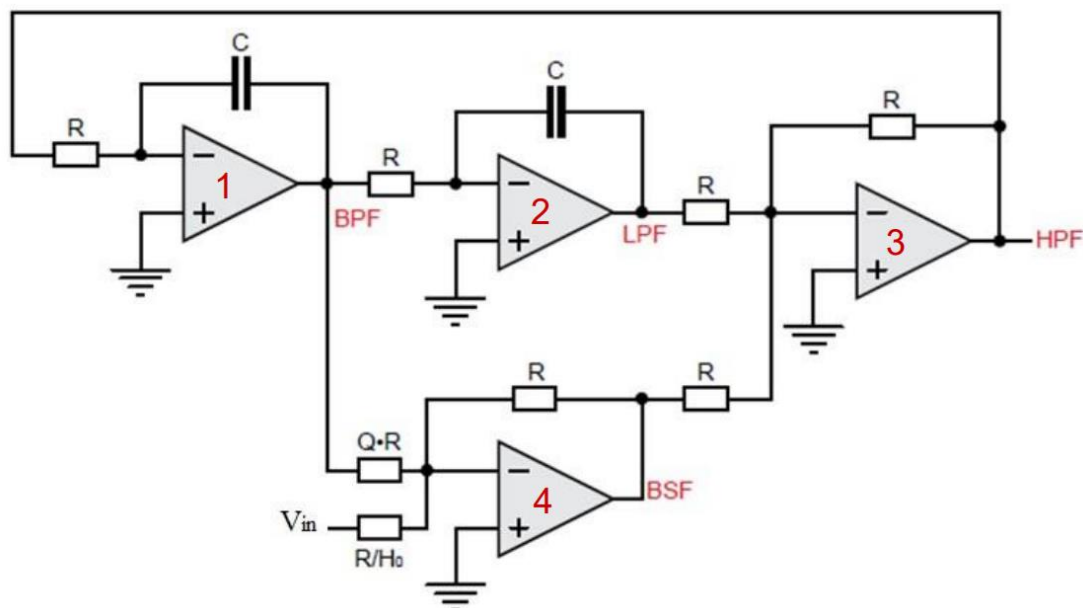

Task 1

Derivations and Parameters

Assume for all Op-amps are ideal and in Negative Feedback $\rightarrow V_{out} = A_v(V_{in}^+ - V_{in}^-)$.

Since the output is Finite, While $A_v \rightarrow \infty$, then $(V_{in}^+ - V_{in}^- = 0) \rightarrow V_{in}^+ = V_{in}^-$

We use KCL at input nodes in S-domain to approach the derivations.

OP - AMP # 1 (BPF)

$$\text{KCL: } \frac{V_{HPF} - 0}{R} = \frac{0 - V_{BPF}}{\frac{1}{SC}}$$

$$\therefore V_{HPF} = -V_{BPF} SCR \rightarrow (1)$$

OP - AMP # 3 (HPF)

$$\text{KCL: } \frac{V_{LPF} - 0}{R} + \frac{V_{BSF} - 0}{R} = \frac{0 - V_{HPF}}{R}$$

$$\therefore V_{HPF} = -V_{LPF} - V_{BSF} \rightarrow (3)$$

OP - AMP # 2 (LPF)

$$\text{KCL: } \frac{V_{BPF} - 0}{R} = \frac{0 - V_{LPF}}{\frac{1}{SC}}$$

$$\therefore V_{BPF} = -V_{LPF} SCR \rightarrow (2)$$

OP - AMP # 4 (BSF)

$$\text{KCL: } \frac{V_{in}}{R/H_o} + \frac{V_{BPF}}{R.Q} = \frac{-V_{BSF}}{R}$$

$$\therefore H_o V_{in} + \frac{1}{Q} V_{BPF} = -V_{BSF} \rightarrow (4)$$

$$\text{From (3): } -V_{BSF} = V_{HPF} + V_{LPF} \text{ , Sub. In (4): } \therefore H_o V_{in} + \frac{1}{Q} V_{BPF} = V_{HPF} + V_{LPF} \rightarrow (5)$$

$$\text{From (2): } V_{BPF} = -V_{LPF} SCR \text{ , From (1): } V_{HPF} = -V_{BPF} SCR$$

Substitute in (5) 4 times to get $H_{LPF}(S)$, $H_{HPF}(S)$, $H_{BPF}(S)$, $H_{BSF}(S)$:

$$H_o V_{in} + \frac{1}{Q} (-V_{LPF} SCR) = -(-V_{LPF} SCR) SCR + V_{LPF} \rightarrow H_o V_{in} = \left(1 + \frac{SCR}{Q} + S^2 C^2 R^2\right) V_{LPF}$$

2nd Order LPF Transfer Function

$$\therefore H_{LPF} = \frac{V_{LPF}}{V_{in}} = \frac{H_o}{S^2 C^2 R^2 + \frac{SCR}{Q} + 1} = \frac{\frac{H_o}{C^2 R^2}}{S^2 + \frac{S}{QCR} + \frac{1}{C^2 R^2}}$$

$$H_o V_{in} + \frac{1}{Q} \left(-\frac{V_{HPF}}{SCR} \right) = V_{HPF} + \frac{-\left(-\frac{V_{HPF}}{SCR} \right)}{SCR} \rightarrow H_o V_{in} = \left(1 + \frac{1}{S^2 C^2 R^2} + \frac{1}{QSCR} \right) V_{HPF}$$

2nd Order HPF Transfer Function

$$\therefore H_{HPF} = \frac{V_{HPF}}{V_{in}} = \frac{H_o}{1 + \frac{1}{S^2 C^2 R^2} + \frac{1}{QSCR}} = \frac{H_o S^2}{S^2 + \frac{S}{QCR} + \frac{1}{C^2 R^2}}$$

$$H_o V_{in} + \frac{1}{Q} V_{BPF} = -V_{BPF} SCR + \frac{-V_{BPF}}{SCR} \rightarrow H_o V_{in} = -\left(\frac{1}{Q} + SCR + \frac{1}{SCR} \right) V_{BPF}$$

2nd Order BPF Transfer Function

$$\therefore H_{BPF} = \frac{V_{BPF}}{V_{in}} = \frac{-H_o}{\frac{1}{Q} + SCR + \frac{1}{SCR}} = \frac{-H_o \frac{S}{CR}}{S^2 + \frac{S}{QCR} + \frac{1}{C^2 R^2}}$$

$$\text{From (3): } V_{BSF} = -\left((-V_{BPF} SCR) + \left(-\frac{V_{BPF}}{SCR} \right) \right) \rightarrow V_{BPF} = \frac{V_{BSF}}{SCR + \frac{1}{SCR}}$$

$$\text{From (4): } H_o V_{in} + \frac{1}{Q} \frac{V_{BSF}}{SCR + \frac{1}{SCR}} = -V_{BSF} \rightarrow -H_o V_{in} = \left(1 + \frac{1}{Q SCR + \frac{1}{SCR}} \right) V_{BSF}$$

2nd Order BSF Transfer Function

$$\therefore H_{BSF} = \frac{V_{BSF}}{V_{in}} = \frac{-H_o}{1 + \frac{1}{QSCR + \frac{1}{SCR}}} = \frac{-H_o \left(S^2 + \frac{1}{C^2 R^2} \right)}{S^2 + \frac{S}{QRC} + \frac{1}{C^2 R^2}}$$

PARAMETERS

H_o : DC gain (The Magnitude response be shifted vertically upwards or downwards by $20 \log |H|$).

Q : Quality factor of filter.

ω_o : Cut - off Frequency, From Transfer function $\omega_o = \left(\frac{1}{RC} \right)$.

BW: Bandwidth of the filter, represent the coefficient of S in denominator of the transfer function

$$BW = \frac{\omega_o}{Q} = \frac{1}{QRC}$$

Components Design

Parameters	Its Values
f_o	1 MHz
Q	2.2
H_o	1
$\omega_o = 2\pi f_o$	$6.283 \times 10^6 \text{ rad/sec}$

$$RC = \frac{1}{\omega_o} = 1.592 \times 10^{-7} \text{ sec} \rightarrow (1)$$

In integrated circuit (IC) design, the values of components are converted into physical area on the chip. For instance, capacitance (C) is measured at ($fF/\mu m^2$), and capacitor sizes commonly ranges between 10 picofarads (pF) with dimensions of ($100 \mu m \times 100 \mu m$) to 100 femtofarads (fF) with dimensions of ($10 \mu m \times 10 \mu m$). For resistors, larger ones amplify thermal noise power, following the equation $S(f) = 4KTR$, where K is Boltzmann's constant, T is temperature in Kelvin, and R is resistance. Conversely, smaller resistors generate higher current and power consumption. Typically, resistors measure in the kilo ohms range.

To Summarize that $C \propto \text{Area}$, $R \propto \frac{1}{\text{Power Consumption}}$, So we take the optimal values of R & C to optain small area and small power consumption

Let the nominal value for $R = 10 \text{ k}\Omega$ and from (1): $C = 15.92 \text{ pF}$.

Components Design	Its Values
R	10 $k\Omega$
C	15.92 pF
R/H	10 $k\Omega$
Q.R	22 $k\Omega$


CADENCE SIMULATION

IDEAL OP - AMP SCHEMATIC


Ideal Op - amp is modeled as a Voltage Controlled Voltage Source (VCVS) with Voltage Gain = 10000 , and with $|V_{out}| < 1$ ($V_{max} = 1, V_{min} = -1$)

Note: Since we don't have any pole. Therefore, we don't need a Buffer Stage as ($R_{out} = 0$).

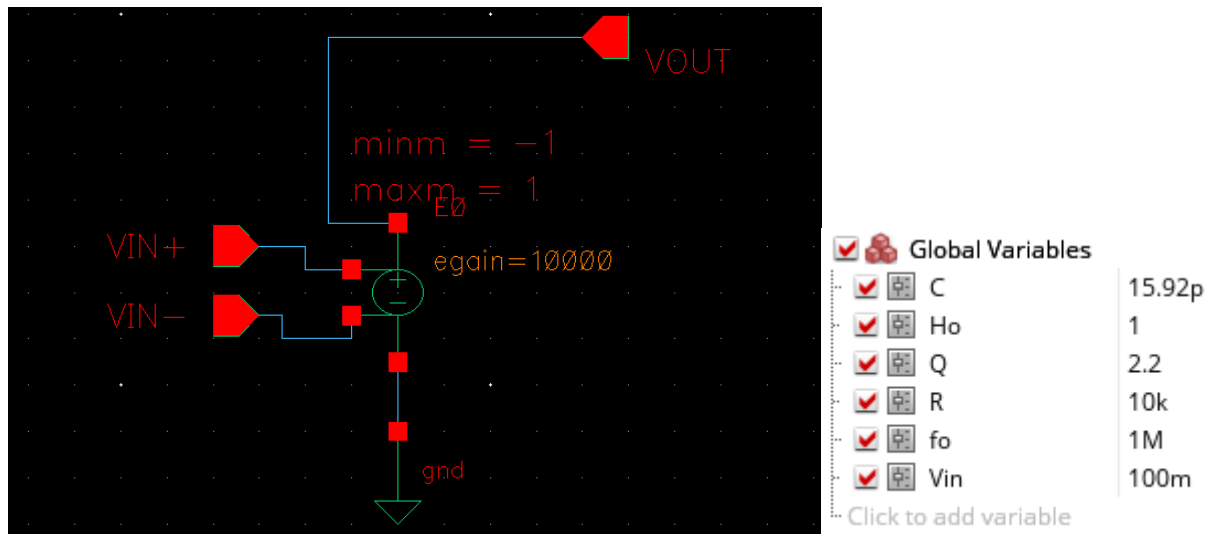Voltage Source is Modeled as a Short Circuit in Small Signal Model.



UNIVERSAL BIQUADRATIC FILTER

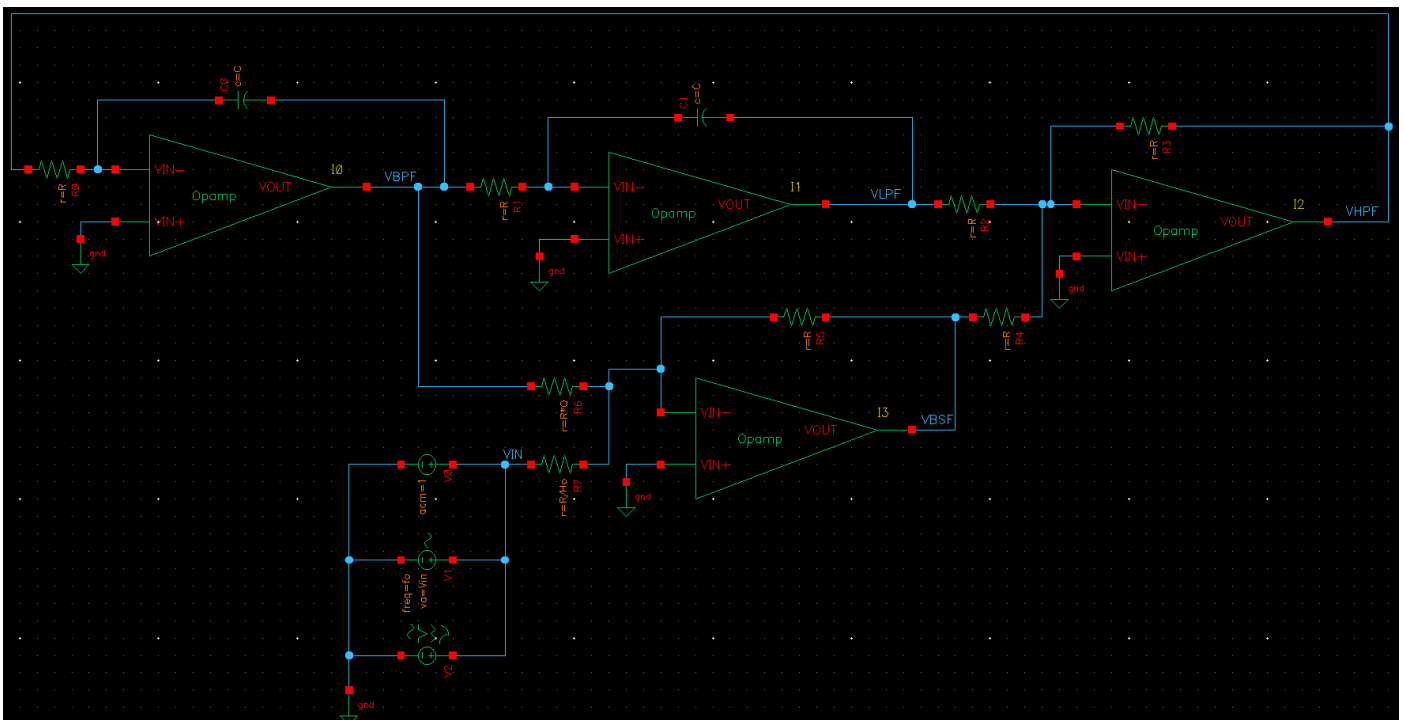

Frequency Response



LPF RESPONSE

Replace ($S = j\omega$), $H_{LPF}(S) = \frac{H_o \omega_o^2}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2} \rightarrow H_{LPF}(\omega) = \frac{\omega_o^2}{(\omega_o^2 - \omega^2) + j\frac{\omega\omega_o}{Q}}$, $|H_{LPF}(\omega)| = \frac{\omega_o^2}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\frac{\omega\omega_o}{Q})^2}}$

For Max Magnitude: $\therefore \frac{d|H(\omega)|}{d\omega} = 0$, $2(\omega_o^2 - \omega^2)(-2\omega) + 2\left(\frac{\omega\omega_o}{Q}\right)\left(\frac{\omega_o}{Q}\right) = 0 \rightarrow \omega_{peak} = \omega_o \sqrt{1 - \frac{1}{2Q^2}}$

Frequency (ω_o) $\omega \rightarrow 0$ $\omega \rightarrow \infty$ $\omega \rightarrow \omega_o \left(H_{LPF}(\omega) = \frac{Q}{j}\right)$ $\omega \rightarrow \omega_{peak} \left(Q > \frac{1}{\sqrt{2}}\right)$

$ H_{LPF}(\omega) $	1	0	Q	$\frac{Q^2}{\sqrt{Q^2 - \frac{1}{4}}} > Q_{slightly}$ $\frac{Q^2}{\sqrt{Q^2 - \frac{1}{4}}} = 2.25 > 2.2$
$\angle H_{LPF}(\omega)$	0°	-180°	-90°	

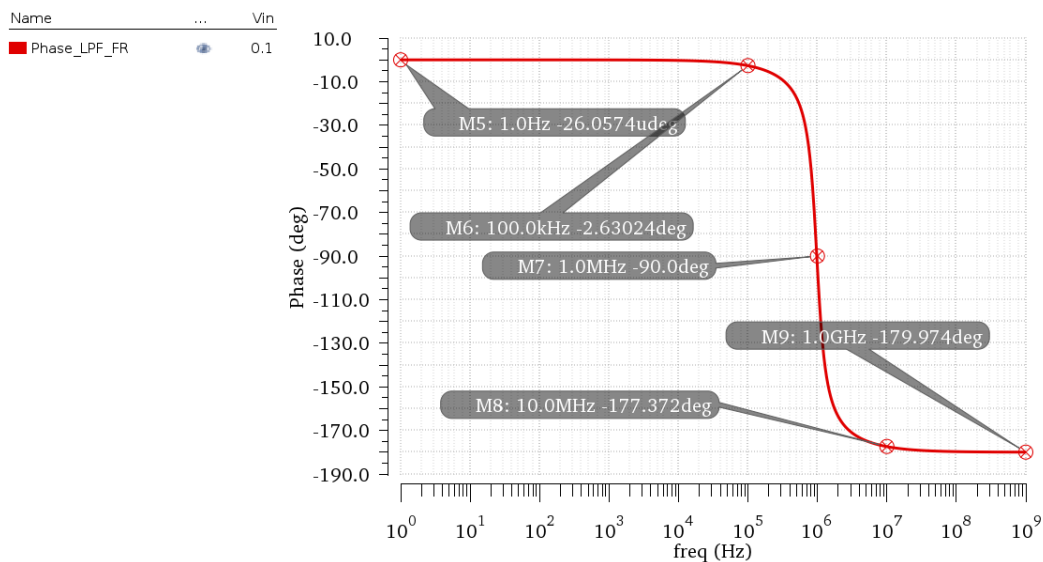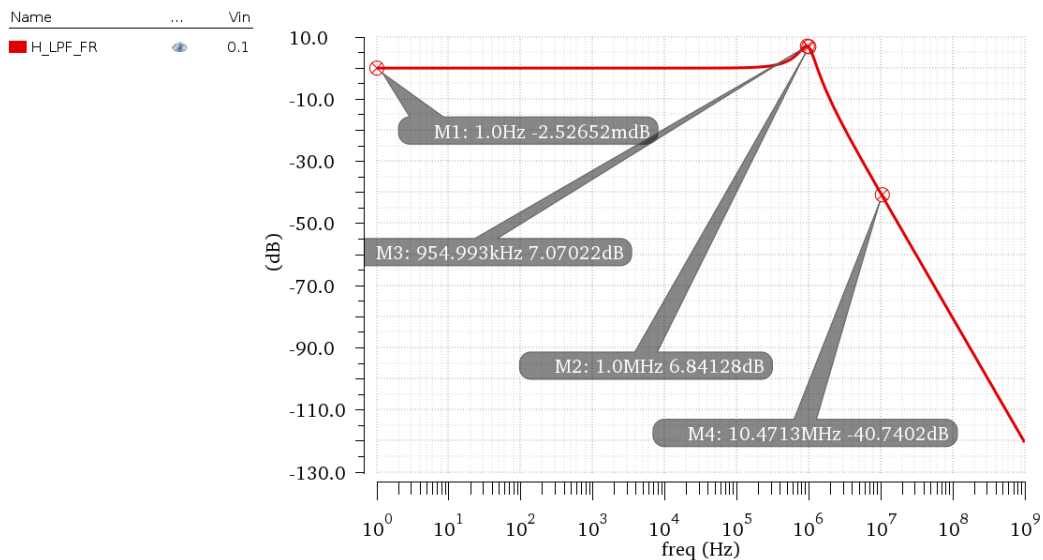


P.O.C	Simulation	Theoretically
Cut off Freq. (ω_o)	From Phase Plot: @ Phase = -90° $f_o = 1 \text{ MHz}$ $\omega_o = 2\pi f_o$ $\omega_o = 6.3 \times 10^6 \text{ rad/sec}$	$C = 15.92 \text{ pF}$, $H_o = 1$, $Q = 2.2$, $R = 10 \text{ k}\Omega$, $\omega_o = \frac{1}{RC} = 6.3 \times 10^6 \text{ rad/sec}$
DC Gain (H)	@ Low Frequency $ H_{LPF}(\omega_{low}) = 20 \log H $ $H_o = 0 \text{ dB} = 1$	$H_o = \left(\frac{10 \text{ k}}{10 \text{ k}}\right) = 1$
Quality Factor	From Magnitude Plot: @ ω_o Cut off Freq. $ H_{LPF}(\omega_o) = H_o Q = 6.84128 \text{ dB}$ $Q = 6.84128 \text{ dB} = 2.198$	$Q = \left(\frac{QR}{R}\right) = \frac{22 \text{ k}}{10 \text{ k}} = 2.2$
Peaking Freq (ω_{peak})	From Magnitude Plot: @ $f_{peak} = 954.993 \text{ kHz}$ $V_{peak} = 7.07022 \text{ dB}$ $V_{peak} = 2.257$	$f_{peak} = f_o \sqrt{1 - \frac{1}{2Q^2}} = 946.94 \text{ kHz}$ $V_{peak} = \frac{Q^2}{\sqrt{Q^2 - \frac{1}{4}}} = 2.259$

HPF RESPONSE


Replace ($S = j\omega$), $H_{HPF}(S) = \frac{H_o S^2}{S^2 + \frac{\omega_o}{Q}S + \omega_o^2} \rightarrow H_{HPF}(\omega) = \frac{-\omega^2}{(\omega_o^2 - \omega^2) + j\frac{\omega\omega_o}{Q}}$, $|H_{HPF}(\omega)| = \frac{\omega^2}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\frac{\omega\omega_o}{Q})^2}}$

Frequency (ω_o)	$\omega \rightarrow 0$	$\omega \rightarrow \infty$	$\omega \rightarrow \omega_o$ ($H_{HPF}(\omega) = \frac{-Q}{j}$)
$ H_{HPF}(\omega) $	0	1	Q
$\angle H_{HPF}(\omega)$	180°	0°	90°

Name ... Vin
☒ H_HP_FFR 0.1

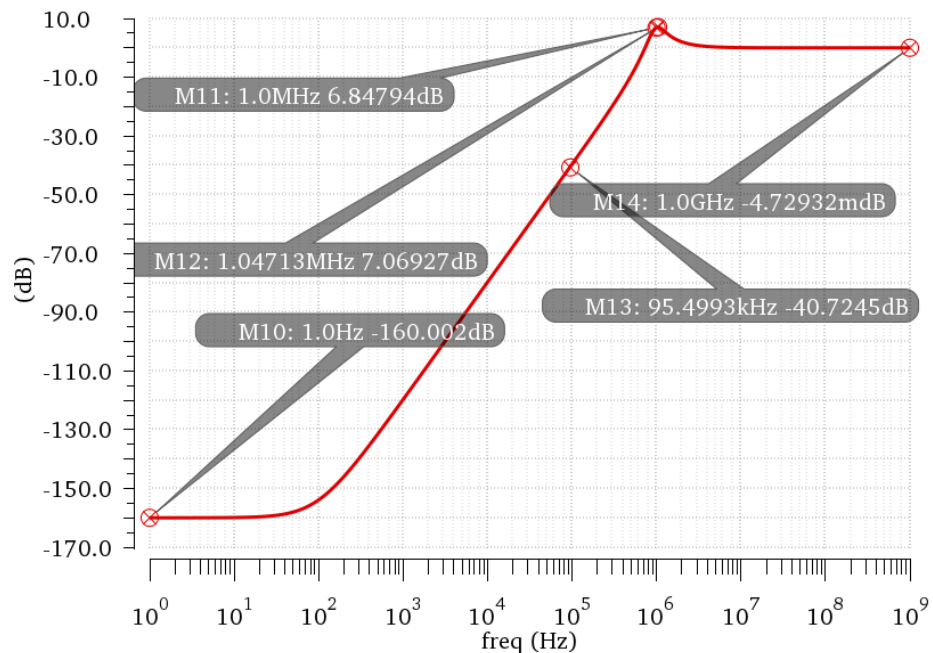

Name ... Vin
 Phase_HPF_FR 0.1

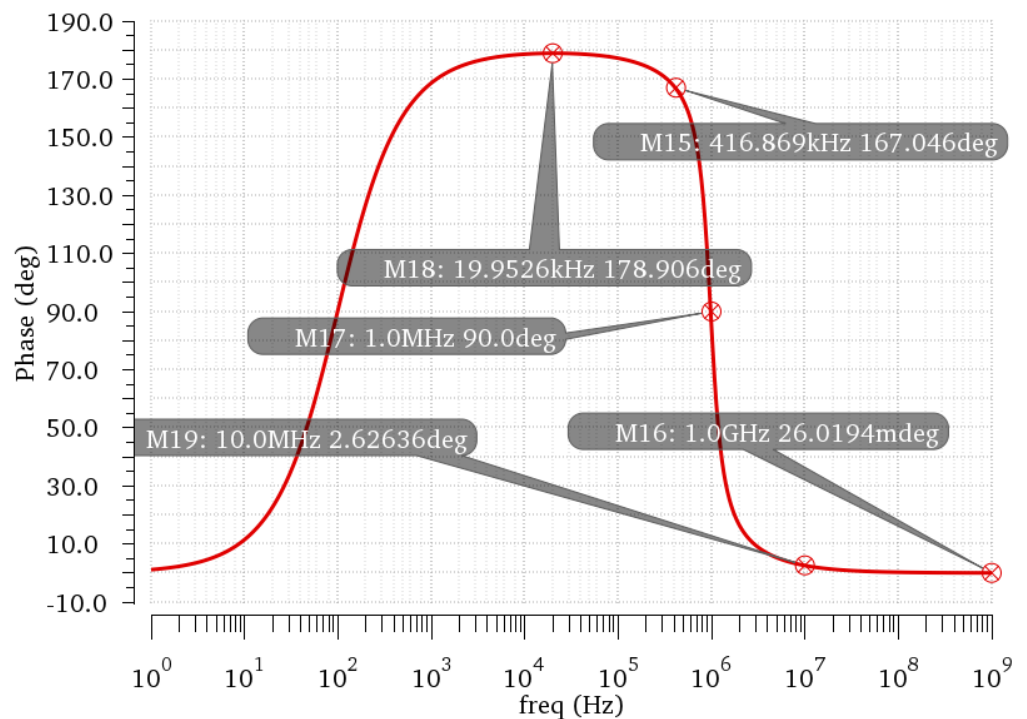

P.O.C	Simulation	Theoretically
Cut off Freq. (ω_o)	From Phase Plot: @ Phase = 90° $f_o = 1 \text{ MHz}$ $\omega_o = 2\pi f_o$ $\omega_o = 6.3 \times 10^6 \text{ rad/sec}$	$C = 15.92 \text{ pF}$, $H_o = 1$, $Q = 2.2$, $R = 10 \text{ k}\Omega$, $\omega_o = \frac{1}{RC} = 6.3 \times 10^6 \text{ rad/sec}$
DC Gain (H)	@ High Frequency $ H_{HPF}(\omega_{infinity}) = 20 \log H $ $H_o = 0 \text{ dB} = 1$	$H_o = \left(\frac{10 \text{ k}}{10 \text{ k}}\right) = 1$
Quality Factor	From Magnitude Plot: @ ω_o Cut off Freq. $ H_{HPF}(\omega_o) = H_o Q = 6.84794 \text{ dB}$ $Q = 6.84794 \text{ dB} = 2.199$	$Q = \left(\frac{QR}{R}\right) = \frac{22 \text{ k}}{10 \text{ k}} = 2.2$
Peaking Freq (ω_{peak})	From Magnitude Plot: @ $f_{peak} = 1.04713 \text{ kHz}$ $V_{peak} = 7.06927 \text{ dB}$ $V_{peak} = 2.257$	$f_{peak} = f_o \sqrt{1 - \frac{1}{2Q^2}} = 946.94 \text{ kHz}$ $V_{peak} = \frac{Q^2}{\sqrt{Q^2 - \frac{1}{4}}} = 2.259$

BPF RESPONSE

Replace ($S = j\omega$), $H_{BPF}(S) = \frac{\frac{\omega_o S}{Q}}{S^2 + \frac{\omega_o}{Q}S + \omega_o^2} \rightarrow H_{BPF}(\omega) = \frac{j\frac{\omega\omega_o}{Q}}{(\omega_o^2 - \omega^2) + j\frac{\omega\omega_o}{Q}}$, $|H_{BPF}(\omega)| = \frac{\frac{\omega\omega_o}{Q}}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\frac{\omega\omega_o}{Q})^2}}$

Frequency (ω_o)	$\omega \rightarrow 0$	$\omega \rightarrow \infty$	$\omega \rightarrow \omega_o$ ($H_{BPF}(\omega) = 1$)
$ H_{BPF}(\omega) $	0	1	1
$\angle H_{BPF}(\omega)$	90°	-90°	0°

@($\omega \rightarrow \omega_{1,2}$ (-3 dBs from peaking))

$$|H_{BPF}(\omega)| = \frac{\frac{\omega\omega_o}{Q}}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\frac{\omega\omega_o}{Q})^2}} = \frac{1}{\sqrt{2}} \rightarrow 2 \left(\frac{\omega\omega_o}{Q}\right)^2 = (\omega_o^2 - \omega^2)^2 + \left(\frac{\omega\omega_o}{Q}\right)^2 \rightarrow (\omega_o^2 - \omega^2)^2 = \left(\frac{\omega\omega_o}{Q}\right)^2$$

$$\omega^2 + \frac{\omega\omega_o}{Q} - \omega_o^2 = 0 \rightarrow \omega_{1,2} = \frac{\pm \frac{\omega_o}{Q} + \sqrt{\left(\frac{\omega_o}{Q}\right)^2 + 4\omega_o^2}}{2} = \pm \frac{\omega_o}{2Q} + \omega_o \sqrt{1 + \frac{1}{4Q^2}}$$


$$\therefore BW = \omega_2 - \omega_1 = \frac{\omega_o}{Q}$$

$$\therefore \omega_o^2 = \omega_2 \omega_1$$


$H_{BPF}(S) = \frac{\frac{\omega_o S}{Q}}{S^2 + \frac{\omega_o}{Q}S + \omega_o^2}$ But The Transfer function is $H_{BPF}(S) = \frac{-H_o Q \left(\frac{S}{RC}\right)}{S^2 + \frac{S}{QRC} + \frac{1}{C^2 R^2}}$

\therefore Magnitude Shifts up by $20 \log|QH_o| \cong 6.848 \text{ dB}$, Phase Shifts down by -180°

Name	...	Vin
■ H_BPF_FR		0.1

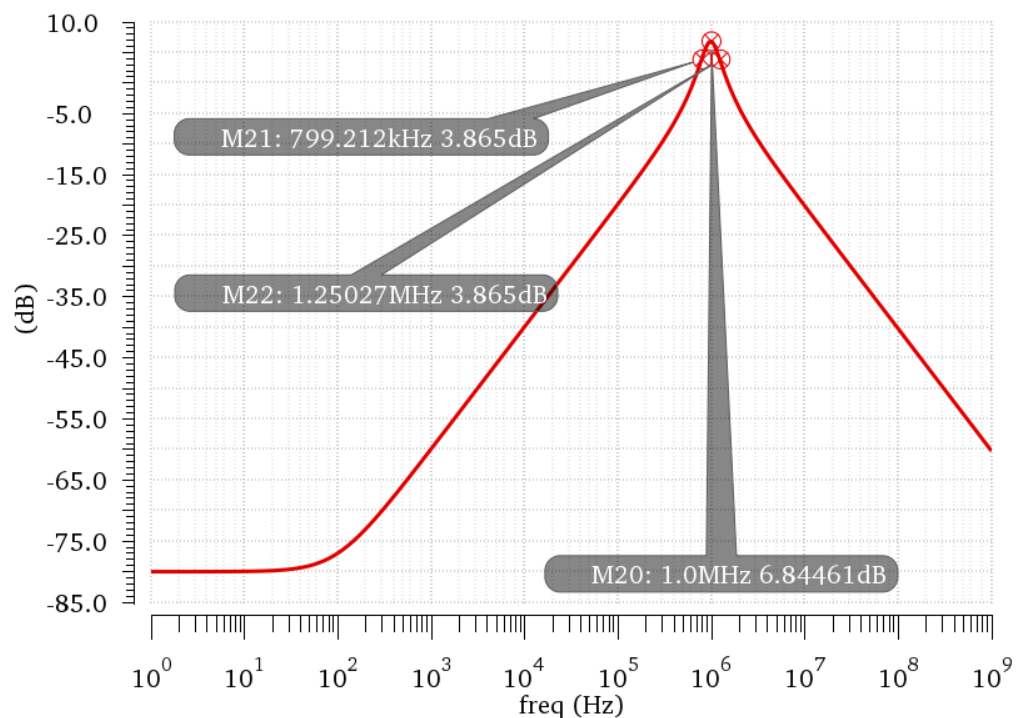

Name ... Vin
 Phase_BPF_FR 0.1

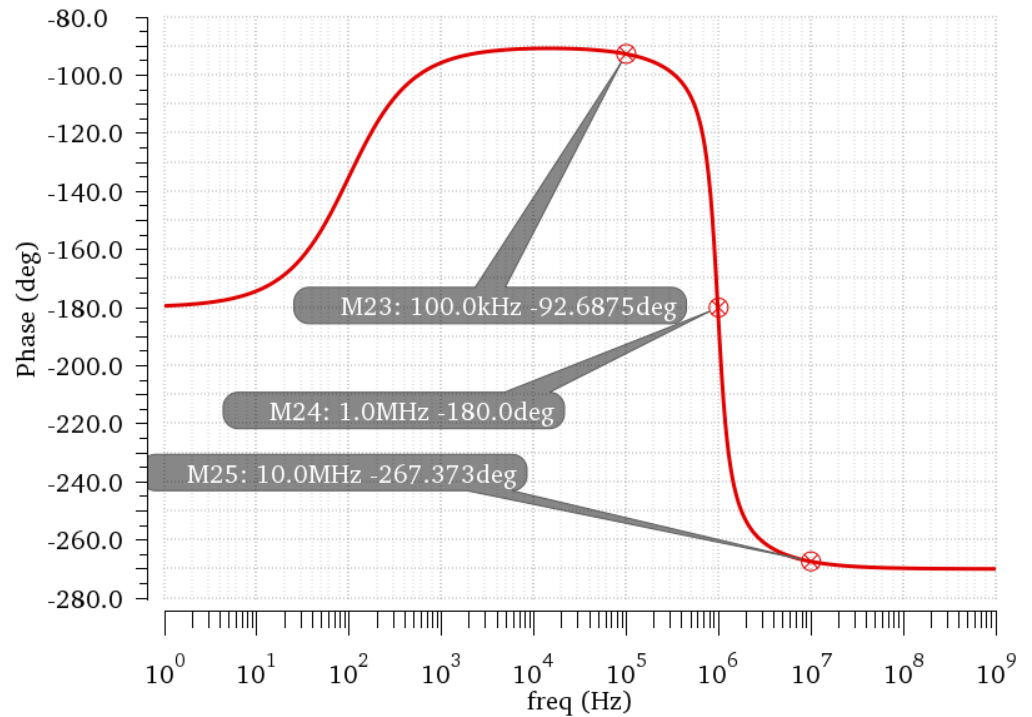

P.O.C	Simulation	Theoretically
Cut off Freq. (ω_o)	From Phase Plot: @ Phase = -180° $f_o = 1 \text{ MHz}$ $\omega_o = 2\pi f_o$ $\omega_o = 6.3 \times 10^6 \text{ rad/sec}$	$C = 15.92 \text{ pF}$, $H_o = 1$, $Q = 2.2$, $R = 10 \text{ k}\Omega$, $\omega_o = \frac{1}{RC} = 6.3 \times 10^6 \text{ rad/sec}$
3 dB $f_{1,2}$	$f_1 = 799.212 \text{ kHz}$ $f_2 = 1.25027 \text{ MHz}$ Note: $\sqrt{f_1 f_2} = 0.99962 \text{ MHz} \cong 1 \text{ MHz}$	$f_{1,2} = \pm \frac{f_o}{2Q} + f_o \sqrt{1 + \frac{1}{4Q^2}}$ $f_1 = 1.253 \text{ MHz}$ $f_2 = 798.23 \text{ kHz}$
DC Gain (H)	From Magnitude Plot: @ ω_o Cut off Freq. $ H_{BPF}(\omega_o) = H_o Q = 6.84461 \text{ dB}$ $20 \log H_o + 20 \log Q = 6.84461 \text{ dB}$ $20 \log H_o = -0.00384 \text{ dB}$ $H_o \cong 1$	$H_o = \left(\frac{10 \text{ k}}{10 \text{ k}}\right) = 1$
Bandwidth BW	$BW = f_2 - f_1 = 451.058 \text{ kHz}$	$BW = \frac{f_o}{Q} = 454.55 \text{ kHz}$
Quality Factor	$Q = \frac{f_o}{BW} = \frac{1 \text{ MHz}}{451.058 \text{ MHz}} = 2.217$	$Q = \left(\frac{QR}{R}\right) = \frac{22 \text{ k}}{10 \text{ k}} = 2.2$

BSF RESPONSE

Replace ($S = j\omega$), $H_{BSF}(S) = \frac{S^2 + \omega_o^2}{S^2 + \frac{\omega_o}{Q}S + \omega_o^2} \rightarrow H_{BSF}(\omega) = \frac{(\omega_o^2 - \omega^2)}{(\omega_o^2 - \omega^2) + j\frac{\omega\omega_o}{Q}}$, $|H_{BSF}(\omega)| = \frac{(\omega_o^2 - \omega^2)}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\frac{\omega\omega_o}{Q})^2}}$

Frequency (ω_o)	$\omega \rightarrow 0$	$\omega \rightarrow \infty$	$\omega \rightarrow \omega_o$	$\omega \rightarrow \omega_o^-$	$\omega \rightarrow \omega_o^+$
$ H_{BSF}(\omega) $	1	1	0	0	0
$\angle H_{BSF}(\omega)$	0°	0°	0°	-90°	90°

@($\omega \rightarrow \omega_{1,2}$ (-3 dBs from peaking))

$$\omega_{1,2} = \frac{\pm \frac{\omega_o}{Q} + \sqrt{(\frac{\omega_o}{Q})^2 + 4\omega_o^2}}{2} = \pm \frac{\omega_o}{2Q} + \omega_o \sqrt{1 + \frac{1}{4Q^2}}$$


$$\therefore BW = \omega_2 - \omega_1 = \frac{\omega_o}{Q}$$

$$\therefore \omega_o^2 = \omega_2 \omega_1$$


$H_{BSF}(S) = \frac{S^2 + \omega_o^2}{S^2 + \frac{\omega_o}{Q}S + \omega_o^2}$ But The Transfer function is $H_{BSF}(S) = \frac{-H_o (S^2 + \frac{1}{C^2 R^2})}{S^2 + \frac{S}{QRC} + \frac{1}{C^2 R^2}}$

\therefore Magnitude Shifts by $20 \log|H_o| \cong 0 \text{ dB}$, Phase Shifts down by -180°

Name	...	Vin
H_BSF_FR		0.1

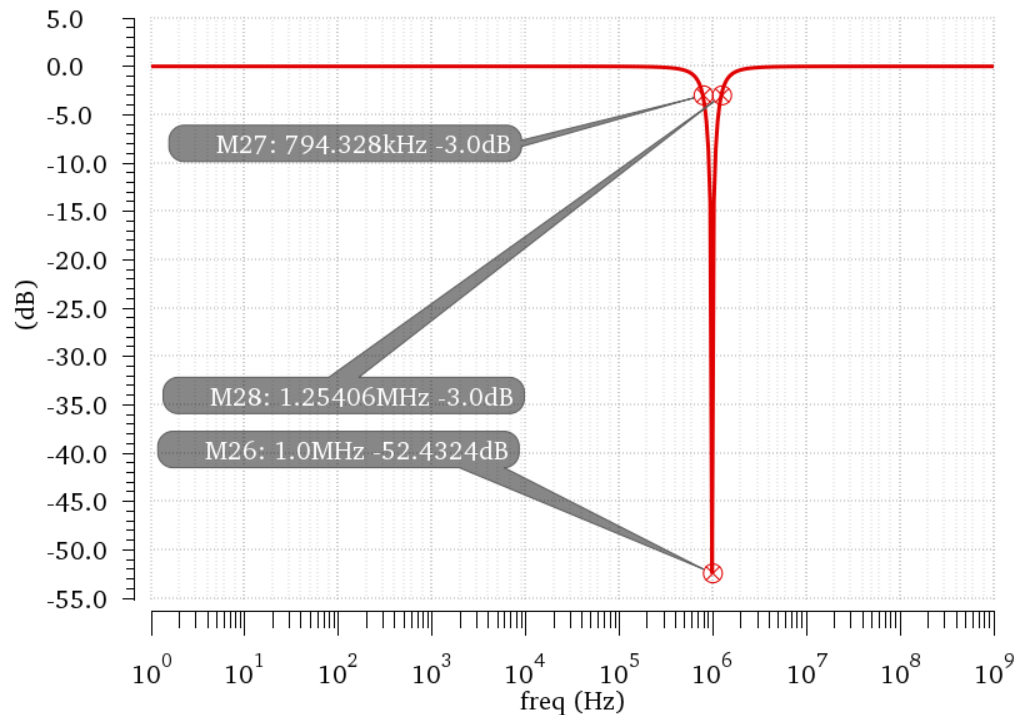


Name ... Vin
 Phase_BSF_FR 0.1

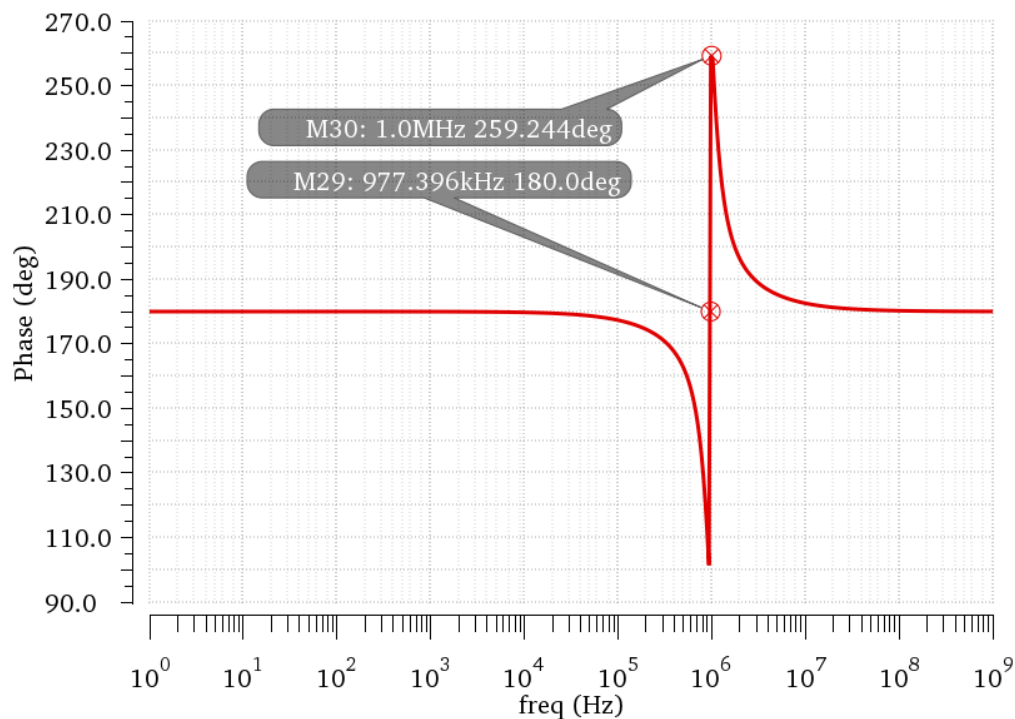


P.O.C	Simulation	Theoretically
Cut off Freq. (ω_o)	From Magnitude Plot @ Notch: @ Magnitude = -52.4324 dB $f_o = 1 \text{ MHz}$ $\omega_o = 2\pi f_o$ $\omega_o = 6.3 \times 10^6 \text{ rad/sec}$	$C = 15.92 \text{ pF}$, $H_o = 1$, $Q = 2.2$, $R = 10 \text{ k}\Omega$, $\omega_o = \frac{1}{RC} = 6.3 \times 10^6 \text{ rad/sec}$
3 dB $f_{1,2}$	$f_1 = 794.328 \text{ kHz}$ $f_2 = 1.25406 \text{ MHz}$ Note: $\sqrt{f_1 f_2} = 0.9981 \text{ MHz} \cong 1 \text{ MHz}$	$f_{1,2} = \pm \frac{f_o}{2Q} + f_o \sqrt{1 + \frac{1}{4Q^2}}$ $f_1 = 1.253 \text{ MHz}$ $f_2 = 798.23 \text{ kHz}$
DC Gain (H)	From Magnitude Plot: @ ω_o Cut off Freq. $ H_{BSF}(\omega_{low}) = H_o = 0 \text{ dB}$ $20 \log H_o = 0 \text{ dB}$ $H_o \cong 1$	$H_o = \left(\frac{10 \text{ k}}{10 \text{ k}}\right) = 1$
Bandwidth BW	$BW = f_2 - f_1 = 459.732 \text{ kHz}$	$BW = \frac{f_o}{Q} = 454.55 \text{ kHz}$
Quality Factor	$Q = \frac{f_o}{BW} = \frac{1 \text{ MHz}}{459.732 \text{ kHz}} = 2.175$	$Q = \left(\frac{QR}{R}\right) = \frac{22 \text{ k}}{10 \text{ k}} = 2.2$

Transient Response Sine Wave
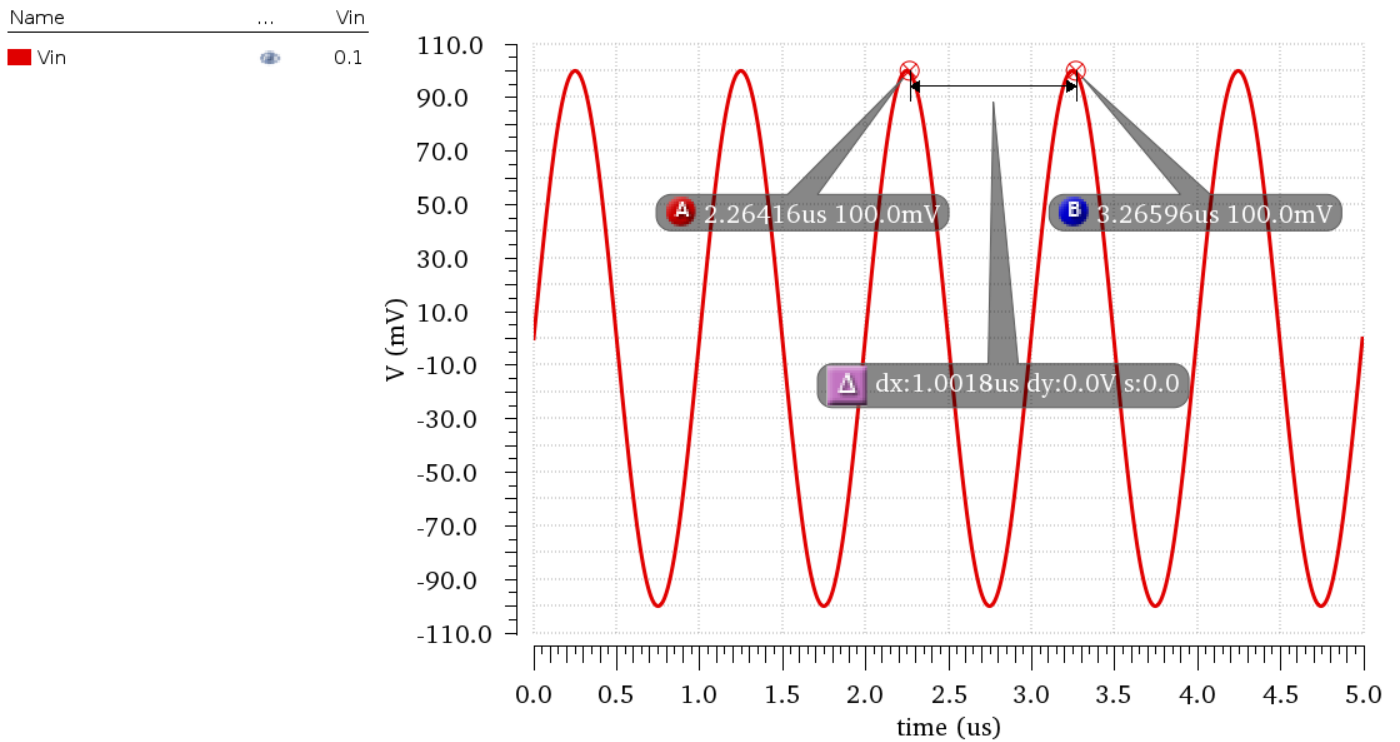
$$V_{sine} (\text{Amplitude} = 100 \text{ mV}, \text{Frequency} = f_o = 1 \text{ MHz}, V_{out} = V_{in} \times H(\omega_o))$$




DFT Analysis For input Sine Wave

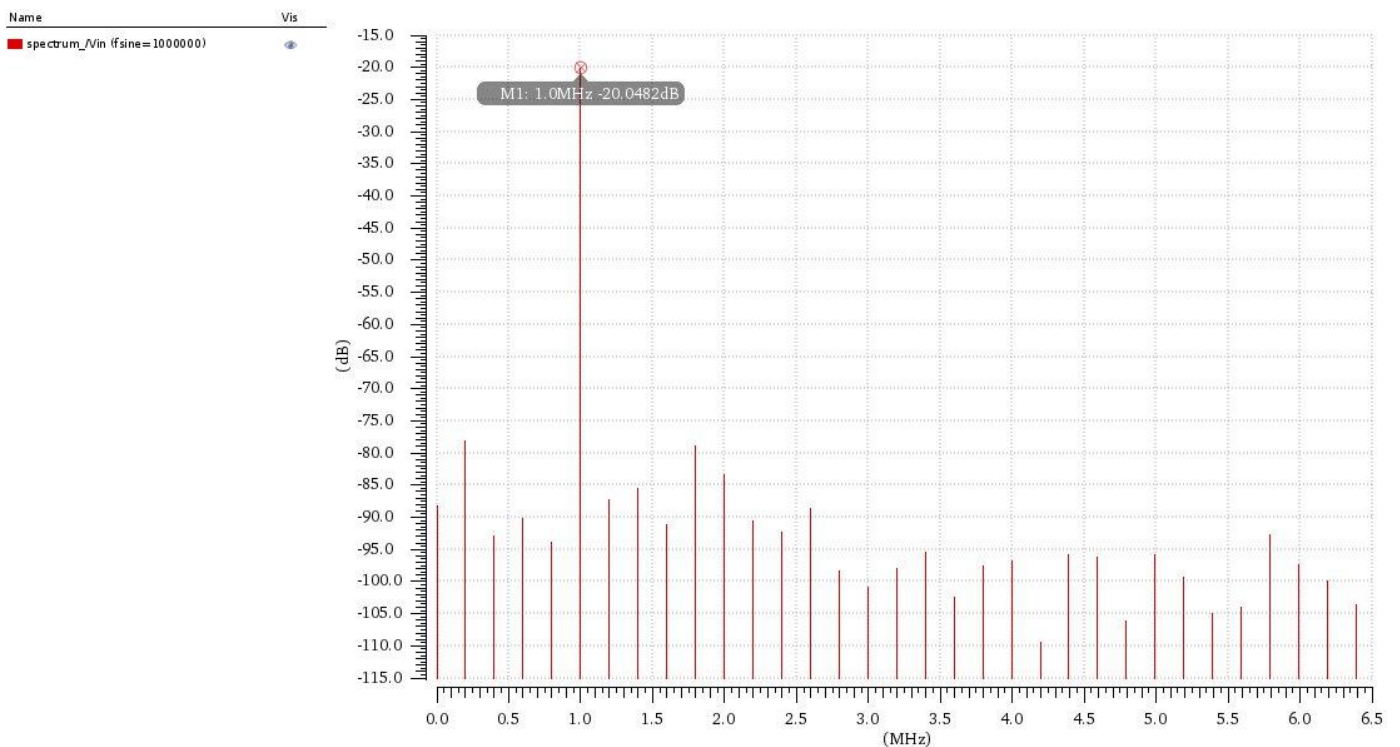


LPF RESPONSE

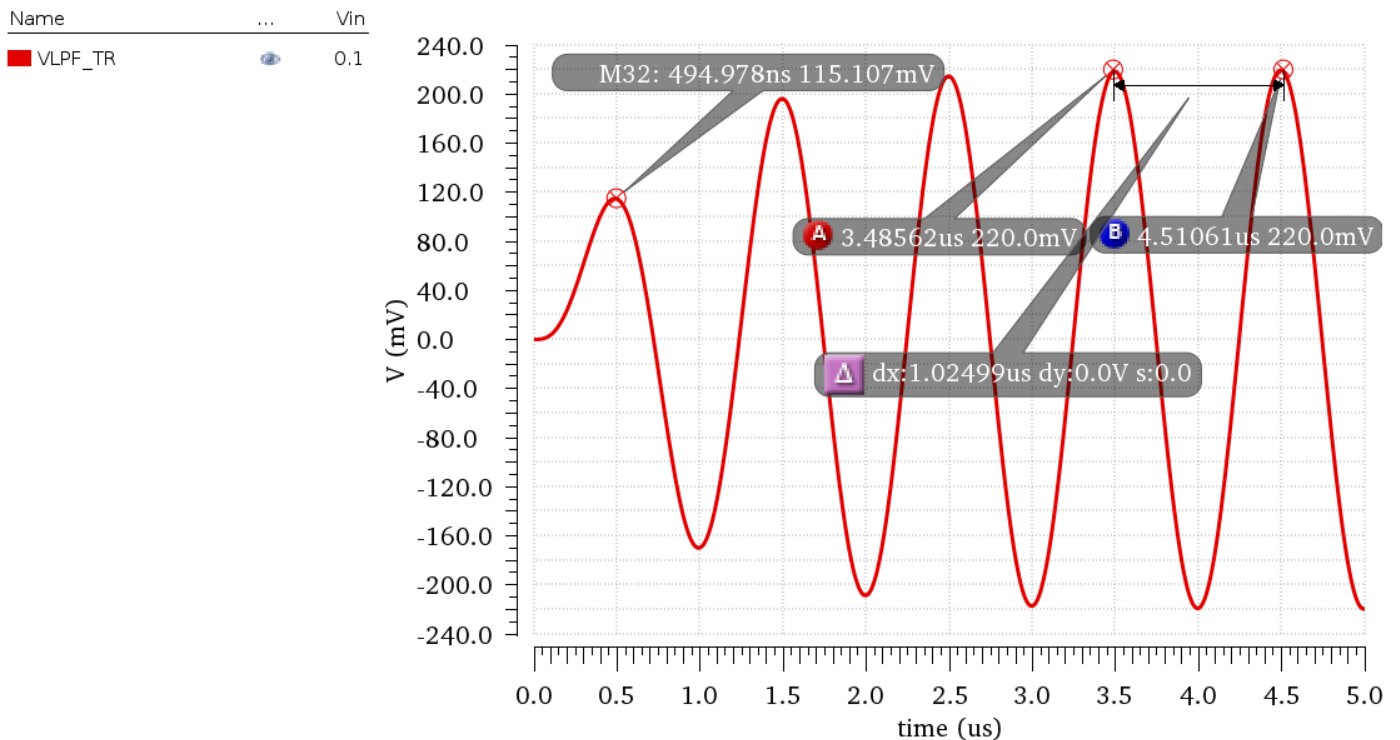LPF Transfer Function for Sine input Waveform in Transient Response




LPF in Transient Response Show the Phase difference
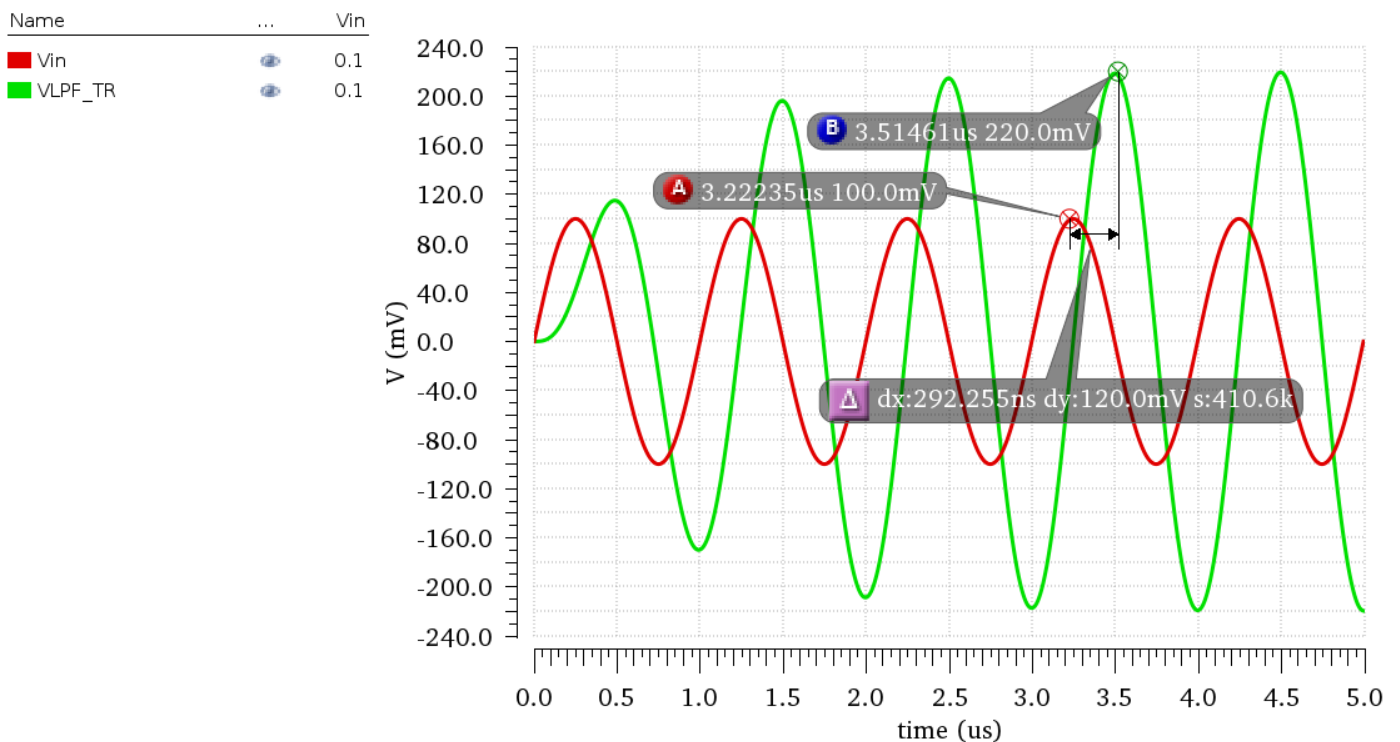
$$\Delta\theta = \frac{\Delta T \text{ (Between I/O peaks)}}{T \text{ (period)}} \times 2\pi = \frac{0.2923 \mu s}{1 \mu s} \times 360^\circ \rightarrow \approx \frac{1}{4} \text{ cycle} \approx -90^\circ$$




LPF DFT Analysis

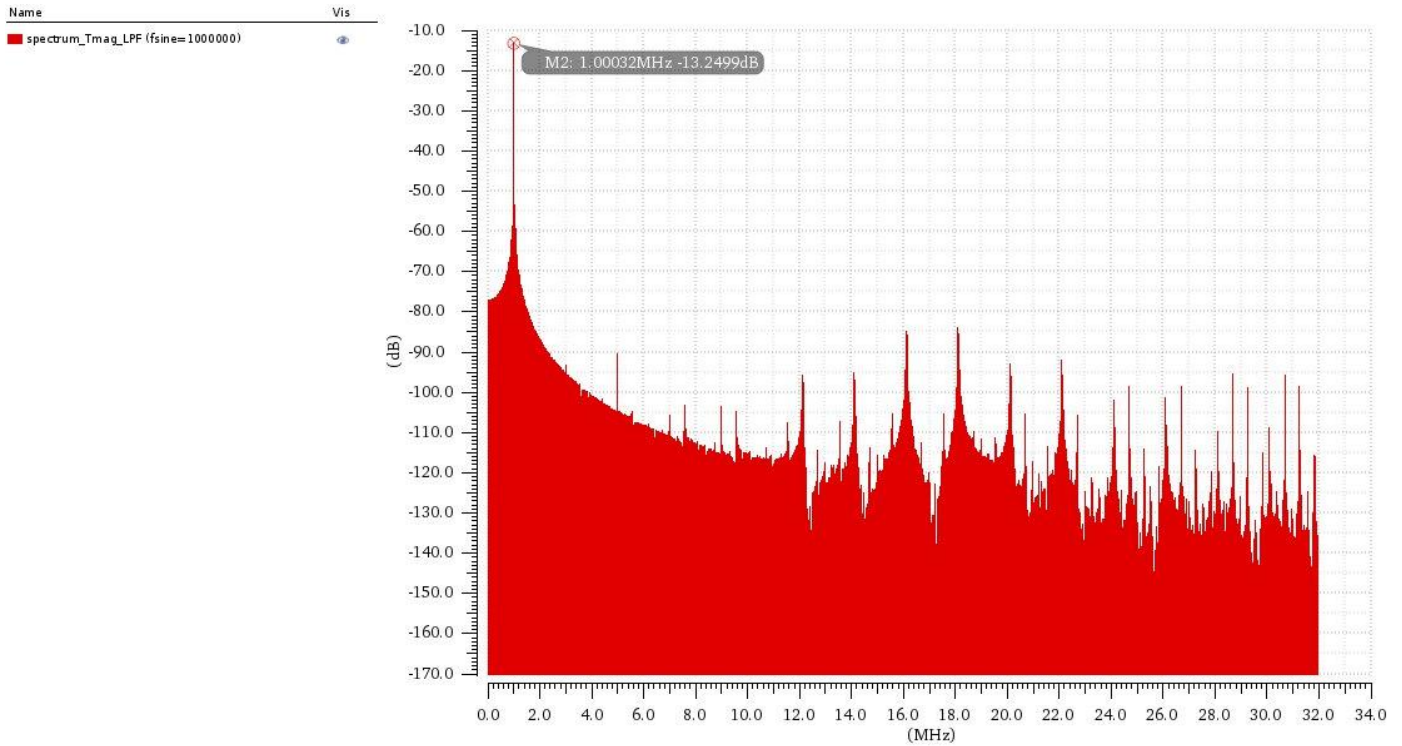

HPF RESPONSE

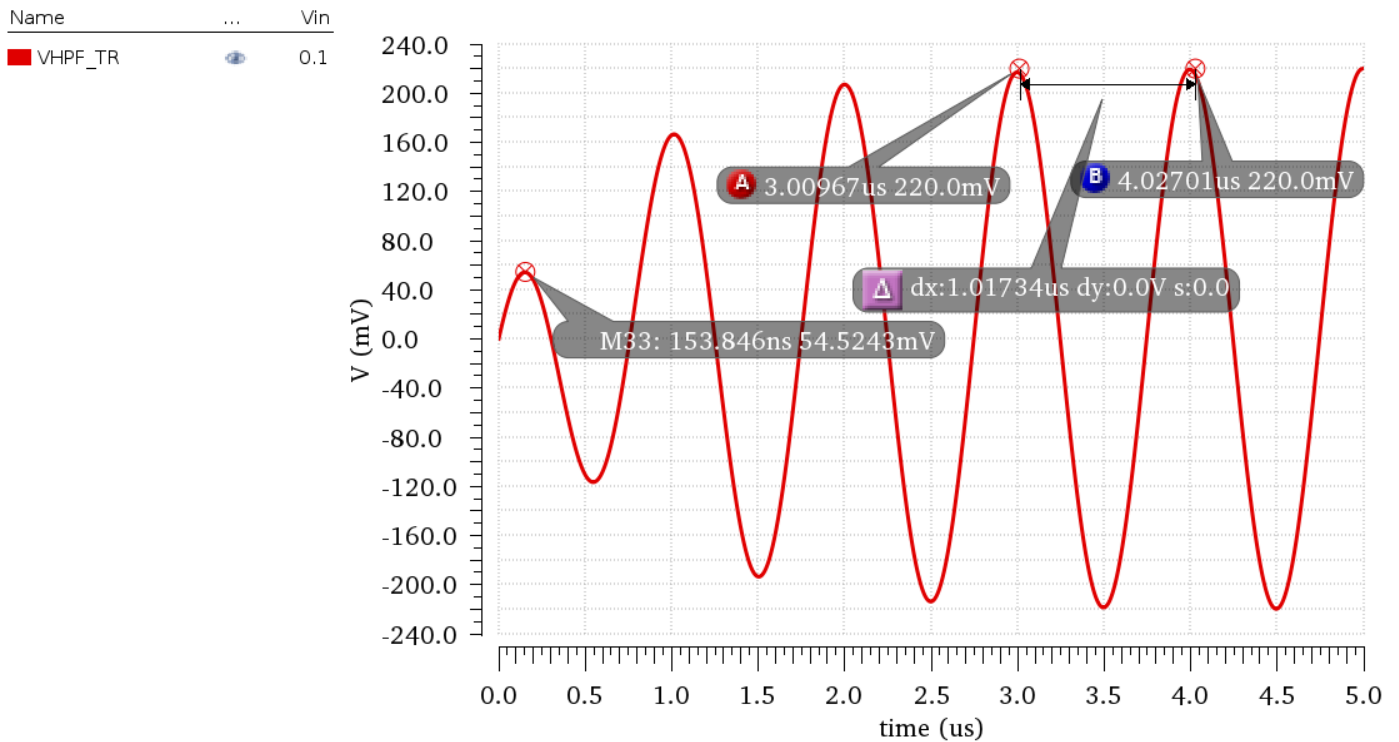
HPF Transfer Function for Sine input Waveform in Transient Response



HPF in Transient Response Show the Phase difference


$$\Delta\theta = \frac{\Delta T \text{ (Between I/O peaks)}}{T \text{ (period)}} \times 2\pi = \frac{0.2273 \mu s}{1 \mu s} \times 360^\circ \rightarrow \approx \frac{1}{4} \text{ cycle} \approx +90^\circ$$

Name	...	Vis
Vin		0.1
VHPF_TR		0.1

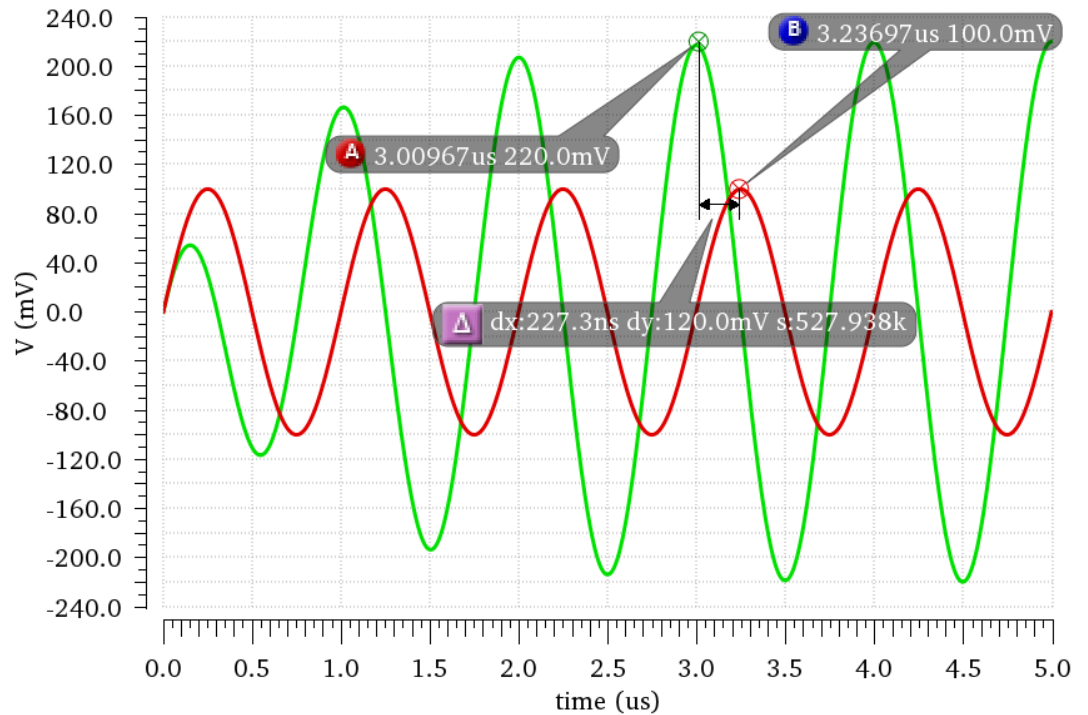

HPF DFT Analysis


Name	Vis
spectrum_Tmag_HPF (fsine=1000000)	

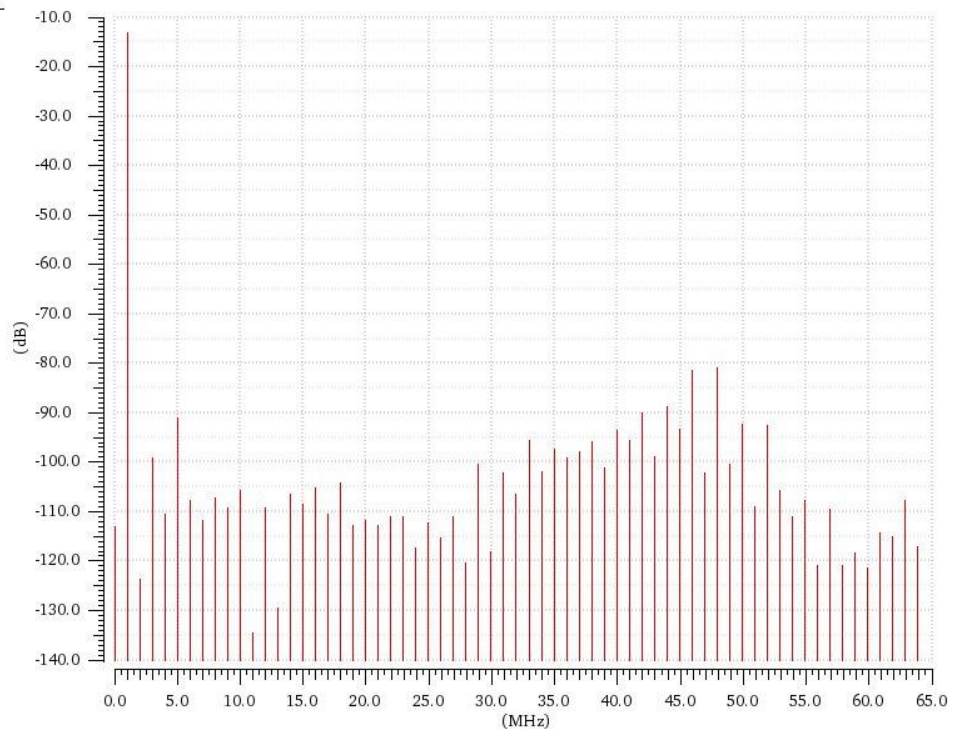


P.O.C	Transient Simulation	AC Simulation
Amplitudes	$V_{in} = 100 \text{ mV}$ $V_{LPF} = 100 \times 2.19283 \text{ mV} = 219.3 \text{ mV}$ $V_{HPF} = 100 \times 2.19433 \text{ mV} = 219.4 \text{ mV}$	$ H_{LPF}(\omega_o) = H_o Q = Q$ $ H_{HPF}(\omega_o) = H_o Q = Q$ $Q = 2.198$ $V_{LPF} = V_{in} \times Q = 219.8 \text{ mV}$ $V_{HPF} = V_{in} \times Q = 219.9 \text{ mV}$
Delay Phase Shift	V_{HPF} and V_{LPF} are 180° Out of Phase V_{in} peak @ $t = 3.23697 \mu s$ V_{LPF} peak @ $t = 3.51461 \mu s$ V_{HPF} peak @ $t = 3.00967 \mu s$ $T_{period} = 1 \mu s \rightarrow \lambda = 360^\circ$ $\Delta T_{peak}(LPF - HPF) = 0.5 \mu s = \frac{\lambda}{2} = 180^\circ$ $\Delta T_{peak}(V_{in} - V_{out}) = 0.25 \mu s = \frac{\lambda}{4} = 90^\circ$	@ ω_o Cut off Freq. $\theta_{HPF} = 90^\circ$ $\theta_{LPF} = -90^\circ$ $V_{HPF} = V_{in} Q \angle 90^\circ$ $V_{LPF} = V_{in} Q \angle -90^\circ$
Comments	V_{HPF} Leads V_{in} by 90° V_{LPF} Lags V_{in} by 90° V_{HPF} Leads V_{LPF} by 180°	Between V_{LPF} and V_{HPF} 180° Phase Difference

Transient Response Square Wave
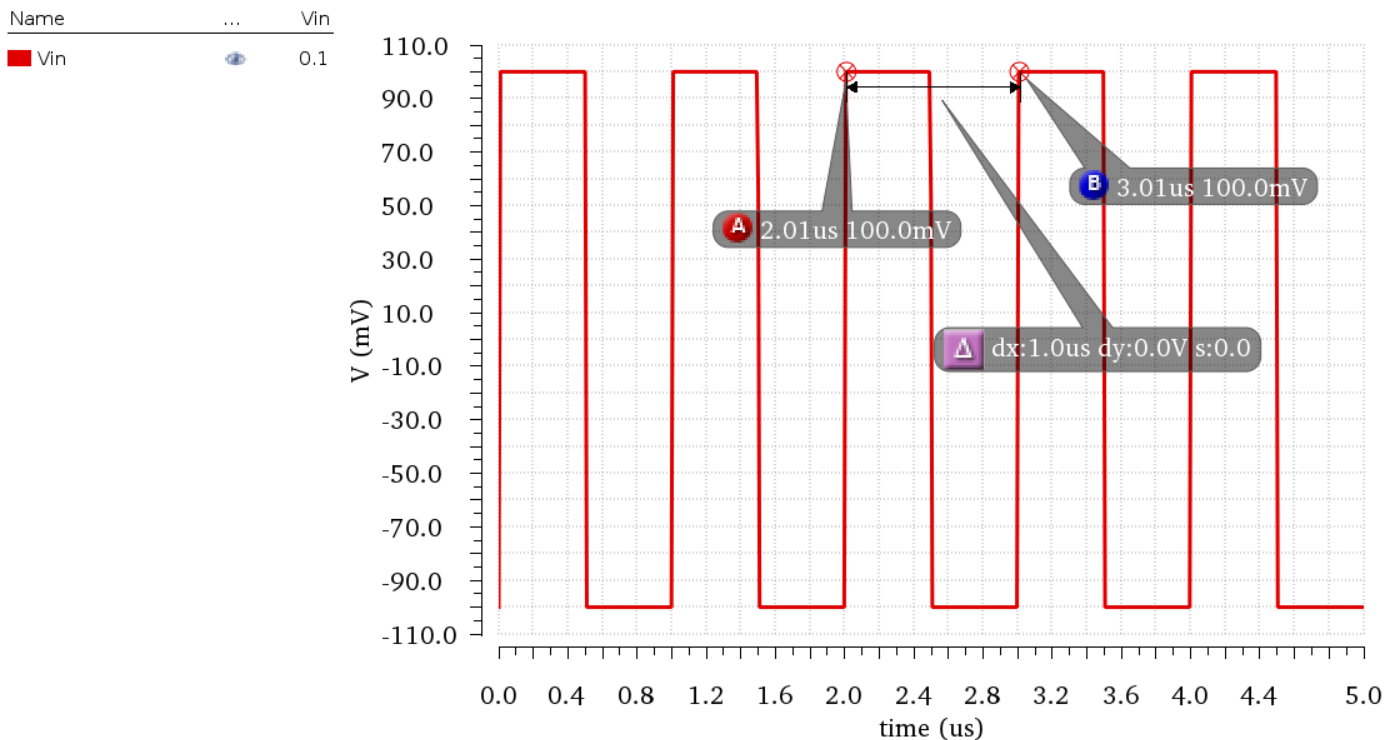
$$V_{source} \text{ Pulse Wave } \left(V_{one} = 100 \text{ mV}, V_{zero} = -100 \text{ mV}, T = \frac{1}{f_o} = 1 \mu s \right)$$




DFT Analysis For input Square Wave

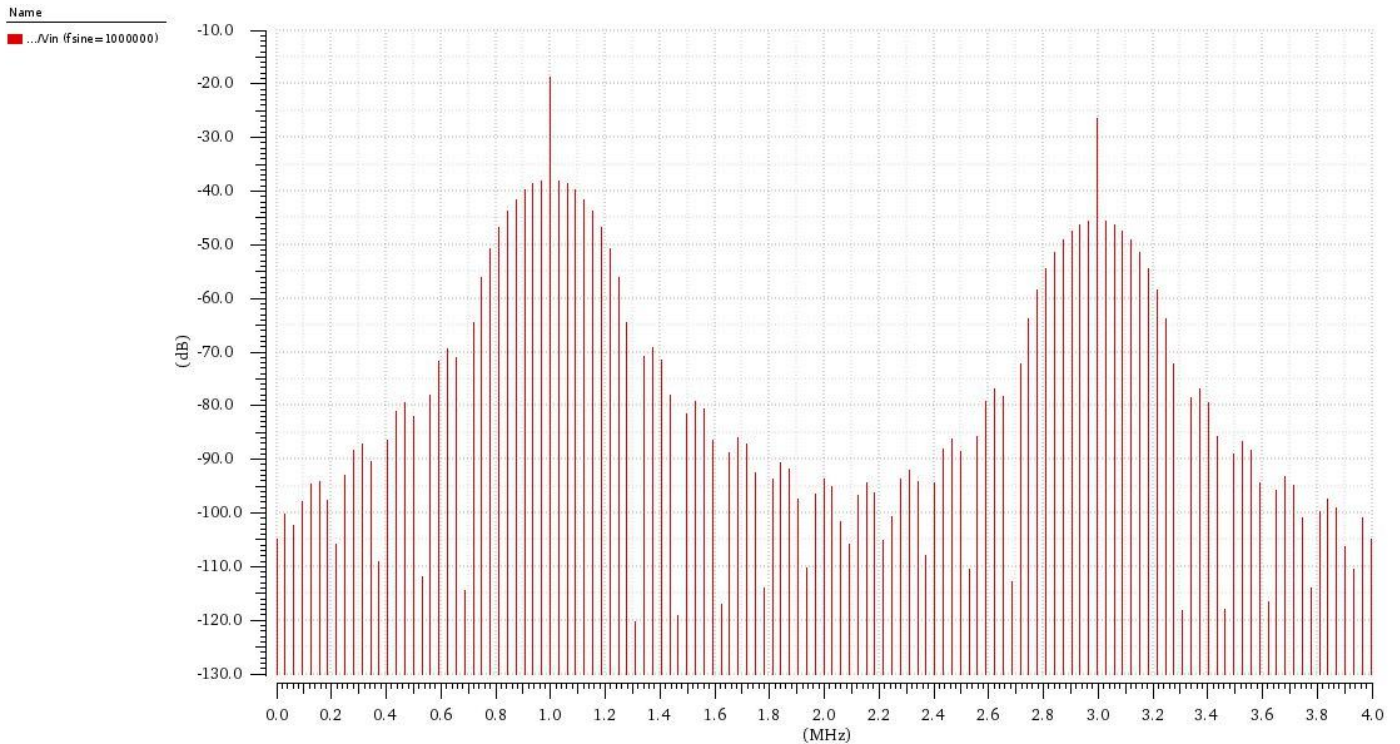


BPF RESPONSE

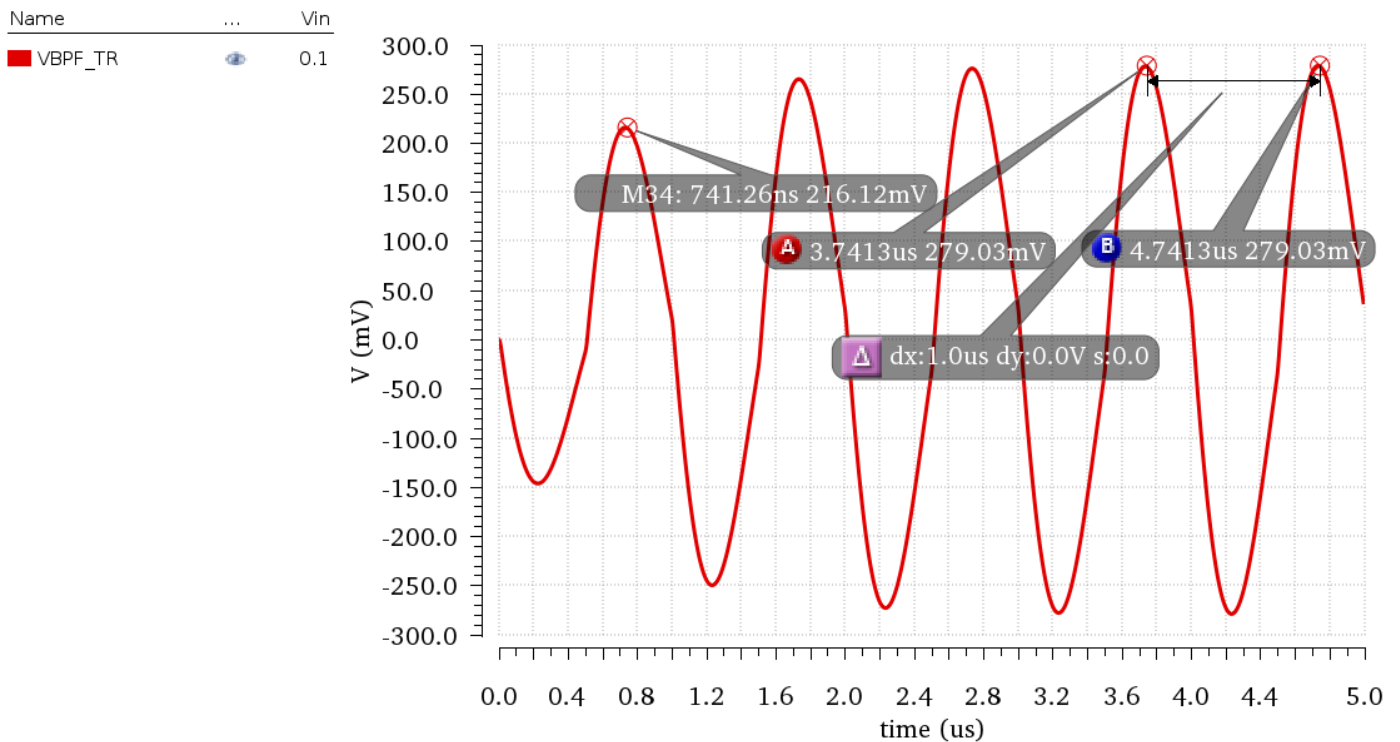BPF Transfer Function for Square input Waveform in Transient Response




BPF DFT Analysis

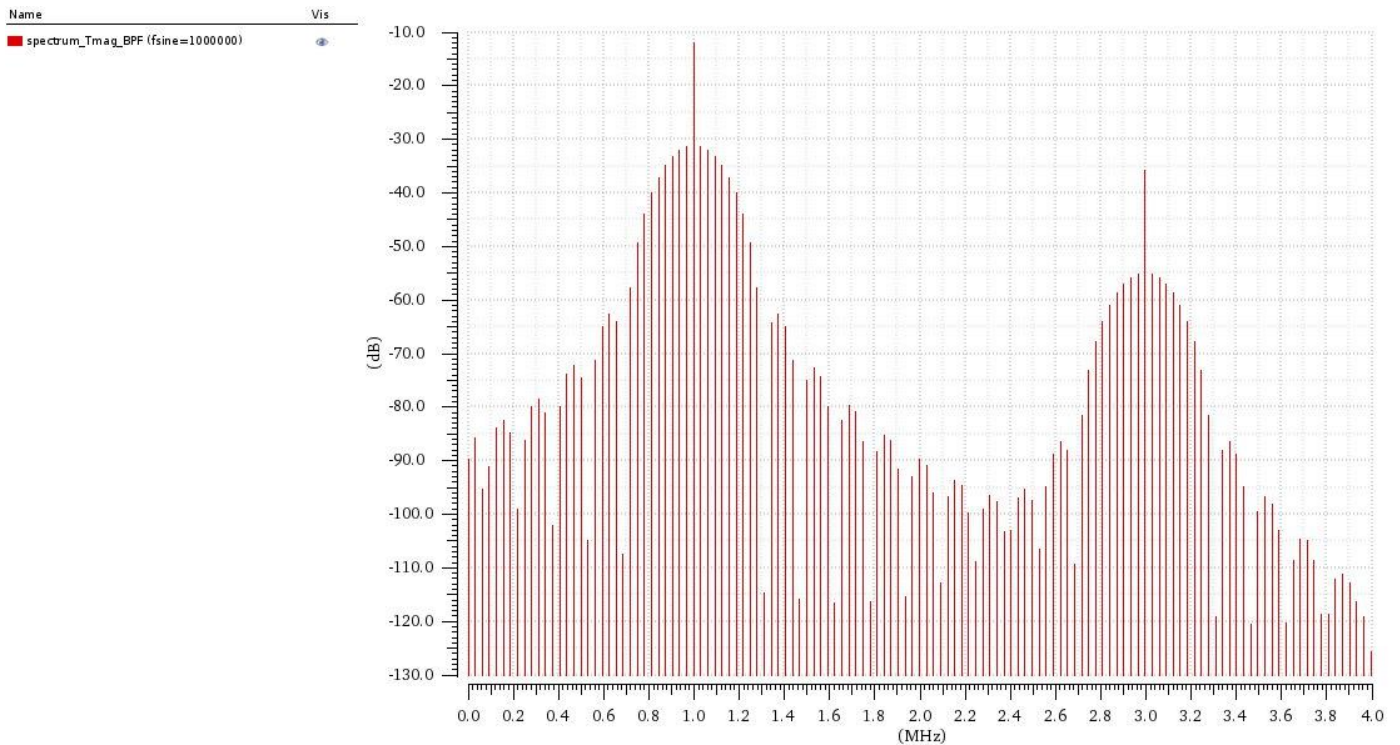(Highest Components is at $f = f_o$ While Other Harmonics get Rejected)




BSF RESPONSE

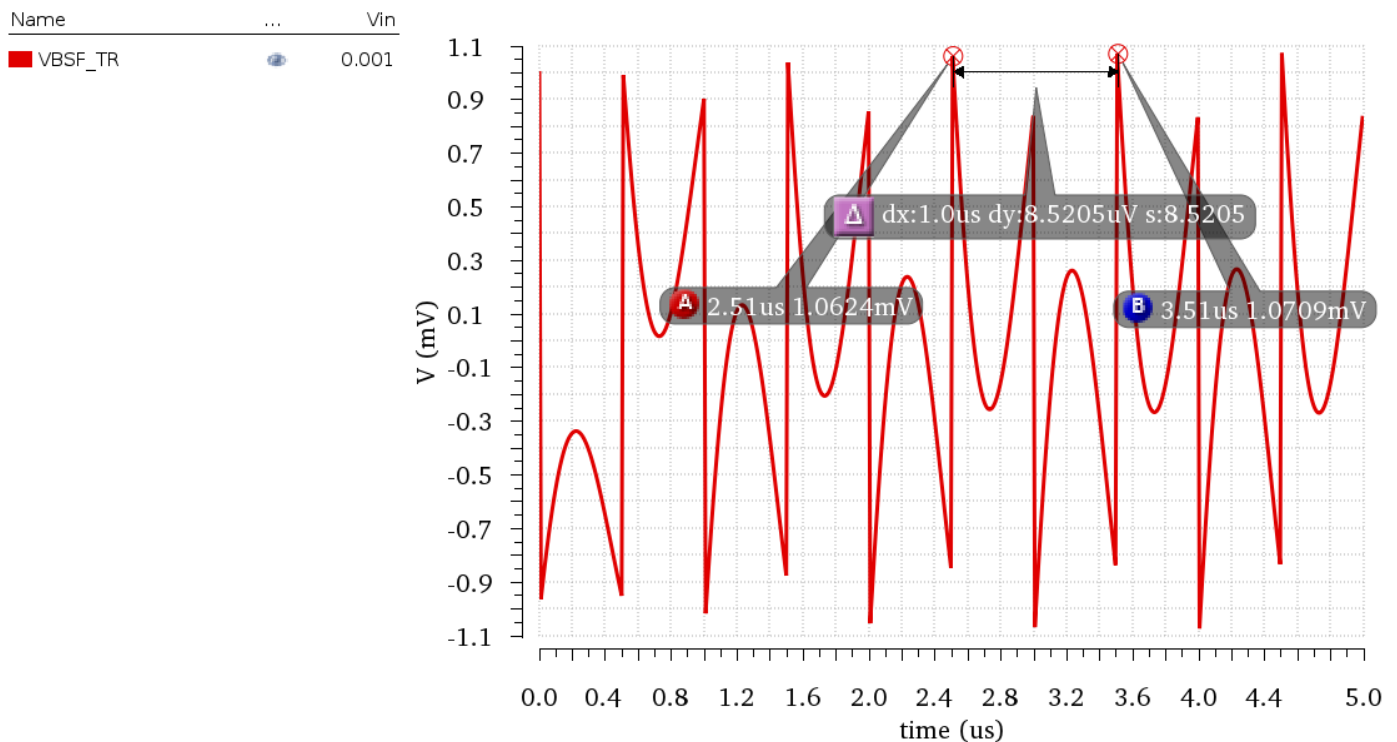BSF Transfer Function for Square input Waveform in Transient Response



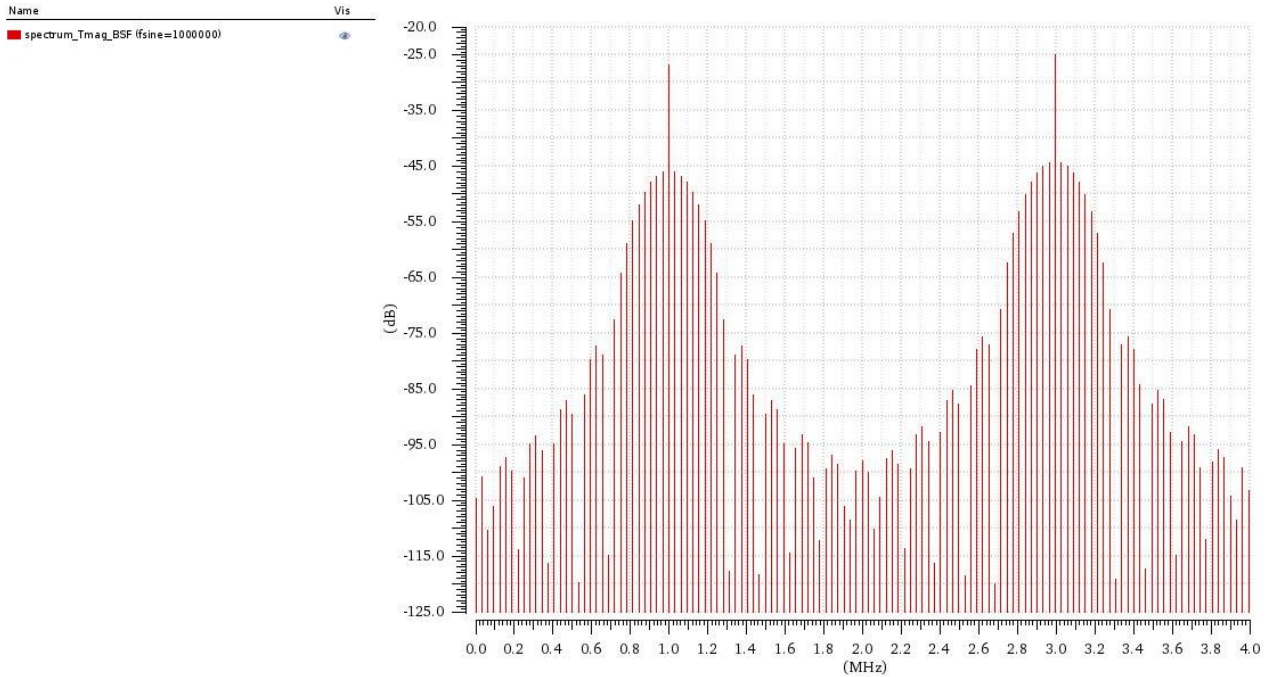BSF DFT Analysis (All Components Seems Rejected Except at $f = f_o$)



COMMENTS

Analysis of Square Pulse Use Fourier Series Coefficient:

$$a_o = \frac{\text{Area}}{T}, b_n = 0 \text{ (even)}, a_n = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} f(t) \sin(n\omega_o t) dt = \frac{2}{n\pi} \sin\left(\frac{n\pi}{2}\right) \text{ (n: odd)}$$

$$V_{in}(t) = 2a_o \left[\frac{1}{2} + \sum \frac{2}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\omega_o t) \right] = 2a_o \left[\frac{1}{2} + \frac{2}{\pi} \left(\cos(\omega_o t) - \frac{1}{3} \cos(3\omega_o t) + \frac{1}{5} \cos(5\omega_o t) - \dots \right) \right]$$

$$V_{out}(t) = 2a_o \left[\frac{1}{2} H(0) + \frac{2}{\pi} \left(\cos(\omega_o t) H(\omega_o) - \frac{1}{3} \cos(3\omega_o t) H(3\omega_o) + \frac{1}{5} \cos(5\omega_o t) H(5\omega_o) - \dots \right) \right]$$

These Frequency Components are (Pass , Amplified , Rejected)

Frequency	BPF	BSF
@ $\omega = 0$	$H_{BPF}(0) = 0$ (Rejected)	$H_{BSF}(0) = 1$ (Pass)
@ $\omega = \omega_o$	$H_{BPF}(\omega_o) = Q$ (Pass and amplified)	$H_{BSF}(\omega_o) = 0$ (Rejected and Blocked)
@ $\omega = 3\omega_o$	$H_{BPF}(3\omega_o)$ (Rejected by Some dB)	$H_{BSF}(3\omega_o) = 1$ (Pass)
@ $\omega = 5\omega_o, \dots$	All Higher Harmonics are Rejected	All Higher Harmonics Pass

Notes:

- **BPF Signal:** Slightly Distorted Sine Wave as BPF amplified Component at $f = f_o$ And Reject the Other Components.
- **BSF Signal:** Rectangular Pulse Subtract a Sine Wave From it as BSF Reject the Component at $f = f_o$ and Pass all Other Components.

The END Thank You